



COMPONENTS IN ELECTRONICS

Keeping the electronics industry informed for 25 years

design | technology | products

| applications | business

Mobile Technology
Why ARM's architecture is becoming
an increasingly popular solution

LED Technology
Keeping thermal runaway
under control

Frequency Control
Looking at the key trends impacting
on high specification oscillators

www.cieonline.co.uk

February 2012

TITAN, Industrial Sensors in Automotive Quality

The logo for EBV chips features the text 'EBV' in white, a blue circular icon with a white cross, and the word 'chips' in orange. The background of the entire page is a close-up photograph of a cracked asphalt surface with a yellow and silver industrial sensor protruding from a hole in the pavement.

EBV  **chips**

Keeping thermal runaway under control

Paul Cheeseman looks at how best to avoid thermal runaway when driving multiple LED strings

An increasingly common method of increasing the light output from a high power LED cluster is to run parallel strings of LEDs from a single constant current source. But this option is not without its hazards.

A typical high power 350mA white LED has a forward voltage (V_f) of about 3.3V, so if a cluster of ten LEDs were required in an application, connecting all the LEDs in series would require a driver capable of delivering at least 33V. If the supply voltage is 24VDC, then an expensive boost converter would be required with all the attendant EMC problems that can create.

Connecting the LEDs as two strings of five wired in parallel requires a higher current 700mA constant current source but only 16.5V output voltage. Thus a low cost buck converter running from 24VDC can be used. The circuit similar to that shown in

batch and sequentially manufactured, the V_f of individual LEDs still has a $\pm 20\%$ tolerance. The tolerances mean that the total forward voltage for each string can be very different and therefore the current mismatch significant (see Figure 2).

In a test using identical SMD LEDs from a single production batch and using 1 Ohm resistors to help balance out the forward voltages, the currents flowing in each string were measured to be 306mA and 394mA. The LED driver was still doing its job of correctly limiting the current to 700mA, but the over-current flowing through the second string was seriously overdriving the LEDs.

Worse, as the LEDs started to get warm, the combined forward voltage of the higher current string started to decrease. This increased the imbalance and more current started to flow through the already



over-driven string. The current through the other string of LEDs reduced as the constant current driver compensated, so they started to cool down and their forward voltage increased.

The net result was thermal runaway with

And this circuit is often given as a recommended application example!

What is required is a way of balancing the currents flowing through the two strings to ensure that they remain approximately equal, even if the combined

Figure 1: Driving multiple LED Strings - a theoretical solution


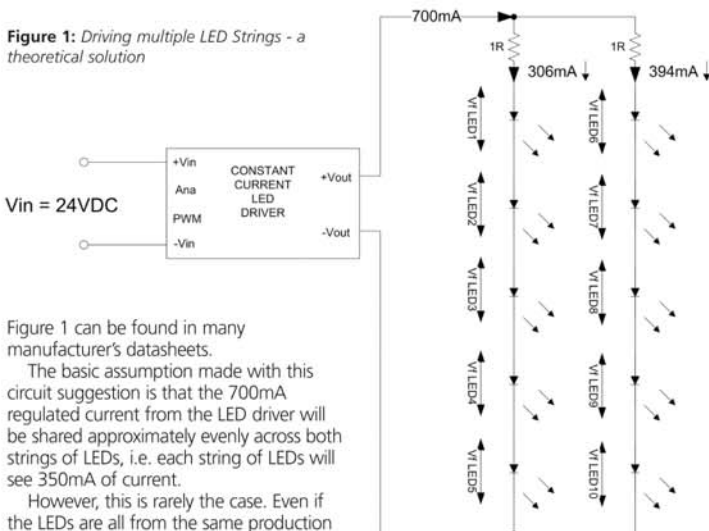


Figure 1 can be found in many manufacturer's datasheets.

The basic assumption made with this circuit suggestion is that the 700mA regulated current from the LED driver will be shared approximately evenly across both strings of LEDs, i.e. each string of LEDs will see 350mA of current.

However, this is rarely the case. Even if the LEDs are all from the same production

Figure 2: Driving multiple LED Strings - Real life situation (not recommended)

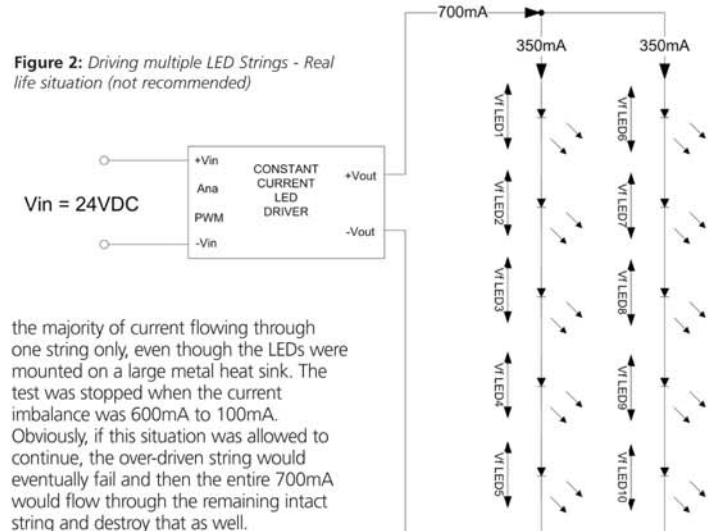

the majority of current flowing through one string only, even though the LEDs were mounted on a large metal heat sink. The test was stopped when the current imbalance was 600mA to 100mA. Obviously, if this situation was allowed to continue, the over-driven string would eventually fail and then the entire 700mA would flow through the remaining intact string and destroy that as well.

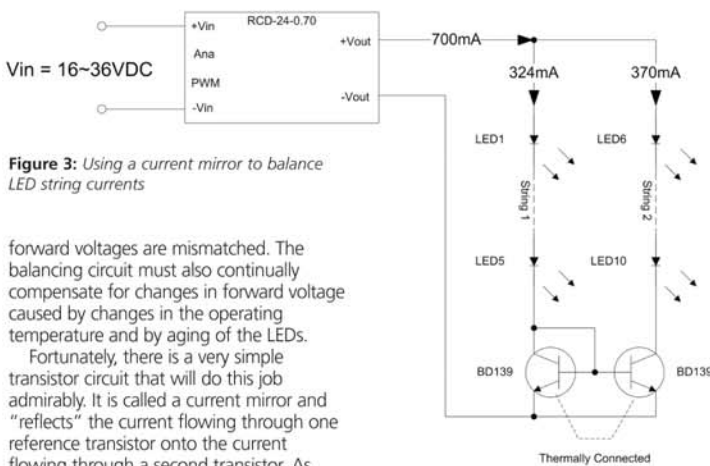


Figure 3: Using a current mirror to balance LED string currents

forward voltages are mismatched. The balancing circuit must also continually compensate for changes in forward voltage caused by changes in the operating temperature and by aging of the LEDs.

Fortunately, there is a very simple transistor circuit that will do this job admirably. It is called a current mirror and "reflects" the current flowing through one reference transistor onto the current flowing through a second transistor. As long as the transistors are reasonably well matched in terms of their V_{be} values, the currents will also be reasonably well matched.

In tests using RECOM's 700mA LED driver and two strings of 350mA Osram LEDs, the currents flowing through the two strings were matched to an accuracy of about 87% over the entire input voltage range of the driver from 16VDC to 36VDC. The LED currents were stable as the LEDs warmed up and no thermal runaway was observed. It is important that the two transistors are both at the same temperature so a copper clamp was used to thermally connect both transistors together to keep their V_{be} voltages stable.

In addition, if any of the LEDs in String 1 fail, the current to ALL of the LEDs is disconnected. Thus the LEDs on String 2 are automatically protected against being over-driven.

However, this circuit is still not ideal. The currents are not perfectly matched and if any of the LEDs in String 2 fail, then all of the 700mA source current will still flow through the first string and destroy it.

Figure 4 shows the final version of the current balancing circuit. The addition of 1.5 Ohm resistors in the emitter paths

makes the circuit less sensitive to small V_{be} changes and balances the currents in the two strings to 99% accuracy.

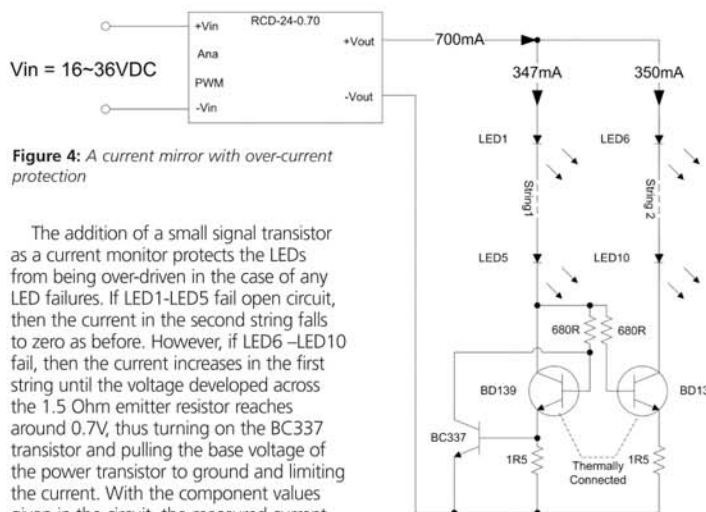


Figure 4: A current mirror with over-current protection

The addition of a small signal transistor as a current monitor protects the LEDs from being over-driven in the case of any LED failures. If LED1-LED5 fail open circuit, then the current in the second string falls to zero as before. However, if LED6-LED10 fail, then the current increases in the first string until the voltage developed across the 1.5 Ohm emitter resistor reaches around 0.7V, thus turning on the BC337 transistor and pulling the base voltage of the power transistor to ground and limiting the current. With the component values given in the circuit, the measured current limit was 445mA with String 2 open circuit.

The circuit suggestion given in Figure 4 can theoretically be extended to any number of LED strings by adding an NPN transistor and emitter resistor to each additional string and tying the transistor bases together. The current flowing through the reference transistor will be faithfully mirrored by all of the other transistors. However, considering that LEDs are high reliability illumination sources and the driver and associated components need to be equally reliable to get the maximum lifetime out of the system, it is recommended that the circuitry be kept as simple as possible and restricted to only one or two strings per driver.

RECOM Electronic
| www.recom-international.com

Paul Cheeseman is Business Development Manager, Sales Northern Europe, RECOM Electronic